



**FIRST TERM THIRD YEAR (5<sup>TH</sup> TERM) B.E.(ELECTRICAL) SUPPLEMENTARY  
EXAMINATION 2012 OF 05 TO 09-BATCHES.**

**INSTRUMENTATION & MEASUREMENT**

Dated: 12-03-2012

Time allowed: 03 Hours.

Max Marks:80

NOTE: ATTEMPT ANY FIVE QUESTIONS. ALL QUESTIONS CARRY EQUAL MARKS.

**Q.No.**

- 01: Describe the difference between indicating, recording and integrating instrument. Give application of each type.
- 02: Explain with the help of neat diagram the construction and principle of operation of single phase induction type energy meter.
- 03: (a) What are the general requirements of shunts and multiplier.  
(b) An ammeter has full scale reading of 1A. it has a resistance of  $1\Omega$ . Calculate the shunt resistance to make it read 2A, 4A and 8A.  
(c) A moving coil instrument has a resistance of  $10\Omega$  and takes 25mA to produce FSD. How can the instrument be adopted to measure (a) voltage up to 120 volts (b) Current up to 20A.
- 04: Describe the electro dynamometer principle. Explain with sketches how the electro dynamometer principle is applied to a volt meter, ammeter and watt meter.
- 05: What are the instrument transformers? Describe briefly.
- 06: Diagram the parts of CRT. Describe how horizontal and vertical deflections can show the wave form on a CRT.
- 07: (a) Draw circuit diagram of Maxwell Wien Bridge and determine an equation which gives its "Condition of Balance".  
(b) At balance the three known impedances of the AC Bridge  
 $Z_1 = 200\Omega$  L 60  
 $Z_2 = 150\Omega$   
 $Z_3 = 100 + j300\Omega$   
Draw the bridge circuit and determine the unknown impedances "ZX" in polar form.
- 08: Write brief notes on any three of the following.
1. Dynamometer type single phase power factor meter
  2. Wheat stone bridge
  3. Electrical resonance frequency meter-ferrodynamic type
  4. Systematic errors
  5. D.C Tachometer Generator

-----THE END-----